 


MIDTERM 2 TOPICS


Building more complicated things!

- Not Gate (Inverter)





if input == 1
output = 0

else
output = 1

 


* Note that for the purposes of these gates we will consider V_{cc} to be 1 and ground to be 0.

NAND Gate

 
 


A	B	out
0	0	1
0	1	1
1	0	1
1	1	0

 


A	B	out
0	0	0
0	1	0
1	0	0
1	1	1

NOR GATE

  



A	B	out
0	0	1
0	1	0
1	0	0
1	1	0

 

A	B	out
0	0	0
0	1	1
1	0	1
1	1	1

OR and AND gates are built with the combination of a NOR or NAND gate and a NOT gate. Therefore, their propagation delays are usually greater.

XOR

  


A	B	out
0	0	0
0	1	1
1	0	1
1	1	0

- Going from a truth table to a circuit:

a	b	c	$f(a,b,c)$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 *Simple way:
We look at the entries the circuit should return 1, then make AND gates corresponding to those entries (marked in red in the example). Then, we OR those.



* We will not cover minimization in this class. If interested, please look up Karnaugh Maps and other related topics.

* Circuit to truth table is simple: try every possible input on the circuit and fill the truth table in.

Boolean Algebra

- Defn: Algebra with boolean operators and binary operands

AND $x \cdot y$ or xy
OR $x + y$
NOT \bar{x}

ORDER OF OPERATIONS

C) first
NOT second (note a large — implies a parenthesis)
AND third
OR fourth

$$a + bc = a + (bc)$$

$$\bar{a}\bar{b} = (\text{not } a) \text{ and } (\text{not } b)$$

$$\overline{ab} = \text{not } (a \text{ and } b)$$

$$a(b+c) = a \text{ and } (b \text{ or } c)$$

Laws

$$\text{Identity Law: } A + 0 = A \quad A \cdot 1 = A$$

$$\text{Zero/one} : A + 1 = 1 \quad A \cdot 0 = 0$$

$$\text{Inverse} : A + \bar{A} = 1 \quad A \cdot \bar{A} = 0$$

$$\text{Commutative} : A + B = B + A \quad A \cdot B = B \cdot A$$

$$\text{Associative} : A + (B + C) = (A + B) + C \quad A(B \cdot C) = (A \cdot B) \cdot C$$

Distributive :


$$A(B + C) = AB + AC$$

$$A + (BC) = (A + B)(A + C)$$

Boolean Algebra \rightarrow Circuits


Each operator is a gate. Simply write the equation out in a circuit.

$$(ab) + (a + \bar{b})$$

 

Circuits to boolean algebra

 - Write out the circuit gates as boolean operators!



$$(ab) + (\bar{a}b)$$

- * Go to truth tables from bool. alg. just as in circuits, plug in all possible inputs, find the correct output.


Propagation Delay

Defn: The delay from time an input signal changes to time the output of the circuit changes to its final "value".


Contamination Delay

Defn: The delay from time an input signal changes to time an output signal changes (note that this refers to ANY change, not the final value).

 A circuit may temporarily produce incorrect output in the red zone below:



 - Gates and wires introduce delays. We will ignore wire delays in this lecture



prop. delay = 20ps
cont. delay = 10ps

* Since NAND and NOR gates are faster than using AND and OR gates, some simple substitutions may make a circuit faster. For this, we rely on this observation:

$$\overline{(a+b)} = \bar{a}\bar{b} \quad \overline{(ab)} = \bar{a} + \bar{b}$$

The above circuit has:

$$\bar{a}b$$

If we replace that with $\overline{(a+b)}$

We lower our prop. delay to 15ps!

Combinational Circuits

Defn: Circuits whose outputs depend **ONLY** on their current inputs.


* No concept of state in a combinational circuit.

ADDITION

a	b	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

↓
XOR


↓
AND

 

1 bit half adder


Full Adder

 - Has additional C_{in} input. Uses 2 Half adders.



1-bit Full Adder

n -bit Adder

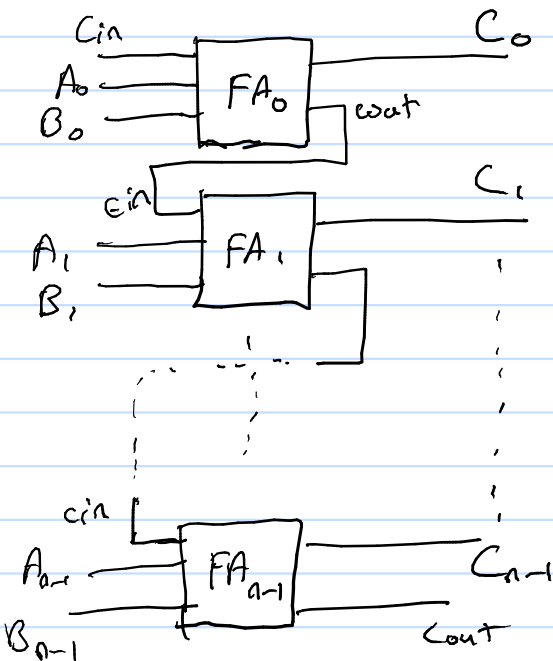

* We can make an n -bit subtractor using an n -bit adder.


Let's observe that

$$A - B = A + (-B)$$

* Which requires negation and addition.
Negation in 2's complement is NOT, +1.
We can do the NOT with a gate,
then use the Cin input of the
final adder to do the +1 part.
The adder will then do subtraction.



* To do both requires a selection.
We select between multiple inputs
with a multiplexer.

 n -bit choice multiplexer with
 m -bit inputs:




Based on the
value of the
choice input,
the MUX outputs
ONLY one of its
inputs.

Adder Subtractor

  

ALU with AND, OR, +, -

 * Note that I'm using a regular adder here.



op_1	op_2	b_{inv}	output
0	0	0	$a b$
0	0	1	$a \bar{b}$
0	1	0	$a + b$
0	1	1	$a + \bar{b}$
1	0	0	$a \text{ AND } b$
1	0	1	$a \text{ SUB } b$
1	1	X	illegal

Additional arithmetic operations

Unsigned overflow detection

- If $Car_{out} = 1$, then there is overflow

2's comp. overflow detection

If most significant bit's $C_{in} \neq C_{out}$, there is overflow. Check with XOR.

Equality checking


A) Do bitwise XOR, then NOR all bits. If 1, they're equal.

B) Subtract numbers, NOR all bits of result. If 1, they're equal.

Set on less than

- Subtract numbers, then the result's most sig. bit is 1 if $a < b$.

n-bit Decoder

 

* Based on in , only ONE of the output wires will be 1, the rest will be 0.

↳ There will always be a wire that is 1!!


Aside: reverse of this is called an encoder

Sequential Circuits

Defn: Circuits whose outputs depend on their current inputs as well as their previous inputs

* These circuits maintain a state!

RS - Latch

 


R	S	Q _s	Q _r
0	0	(memory)	
0	1	1	0
1	0	0	1
1	1	0	0

↙
this entry can't
be remembered!

* Set ONE of the inputs to write a value, then switch both inputs to 0 to remember.

* Mixes WHAT changes and WHEN it changes.

D-Latch

 


D	C	\bar{Q}	Q
0	0	(memory)	
0	1	0	1
1	0	(memory)	
1	1	1	0

* D controls WHAT the state should be

* C controls WHEN it should change.



Clear distinction!

D-latch timeline

 


Q only changes when C is 1


D-flip flop

  

 - Q_s only changes when the clock is falling!
- Q_m changes when $C=1$
- Very brief window where change can happen.
- If the ~~Don~~ is relocated to C_m 's input, then Q_s will change when clock is rising and Q_m will change when $C=0$.




falling edge
D flip flop

 


rising edge
D flip flop


Registers

 

n -bit register

 


Sample MIPS Datapath

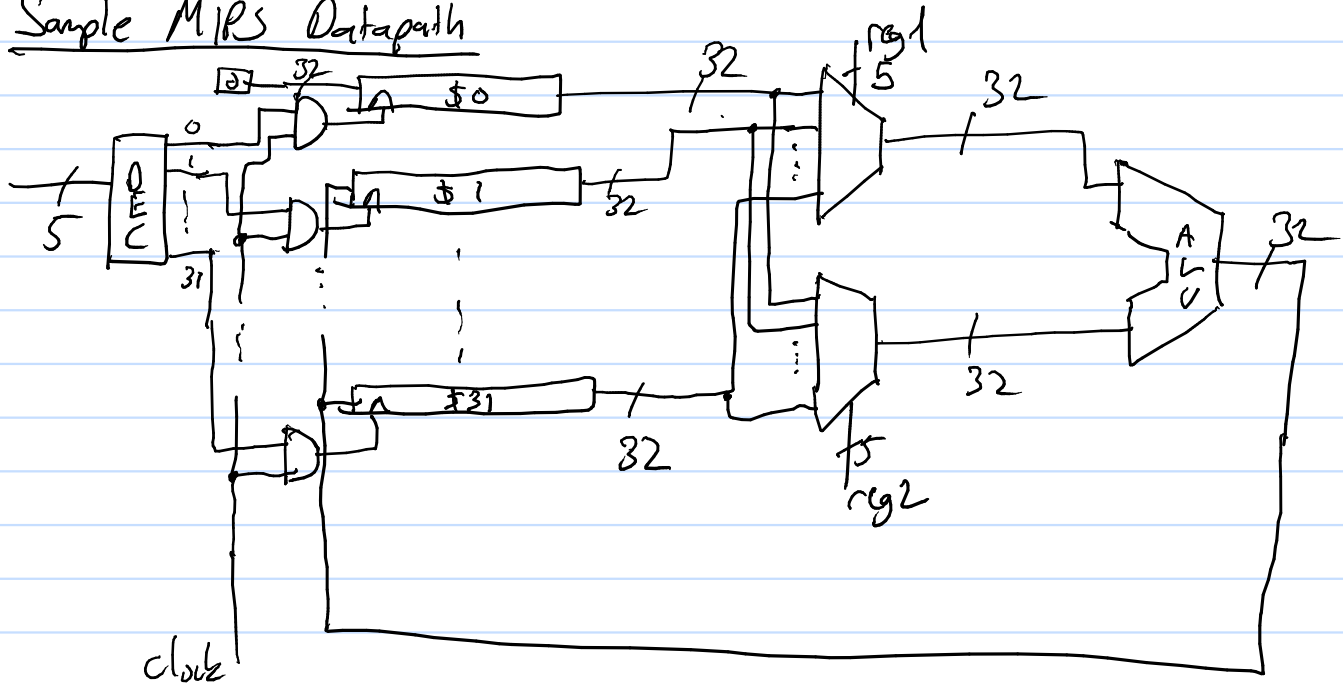

State Machines

* Consists of:

 - 1) A register to hold state
- 2) A comb. circuit to determine output based on state
- 3) A comb. circuit to determine next state based on input and current state.



States are represented with circles. Outputs are in states. Transitions are marked with input.

- 1) We need a 2 bit register to hold state.

2) our output function is:

q_1	q_0	out
0	0	0
0	1	1
1	0	0
1	1	1

3) Our next state function is

q_1	q_0	in	q_{1n}	q_{0n}
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

Memory

Random Access Memory

* Random means we can access any memory word we want in the same amount of time as any other word.

2 major types we will look at:

Static RAM (SRAM)

- ↳ Made from latches

- ↳ Remembers data as long as power is on


Dynamic RAM (DRAM)

- ↳ Stores data in capacitors

- ↳ Forgets data when read or after some time

- ↳ Much, much cheaper than SRAM.

Tri-State Gate

 


control	in	out
0	0	hi-Z
0	1	hi-Z
1	0	0
1	1	1

hi-Z is high impedance

↳ Means there's no charge at all on the wire.


↳ useful for connecting a bunch of outputs without using gates or risking short-circuits

SRAM Cell

 

To Read: wordline = 1, observe bitline
To Write: wordline = 1, charge and hold both bitline & bitline

 - The wordline serves as an enable switch.
- We can represent an SRAM cell like so:



$C=1$ to write
 $E=1$ to read

$n \times m$ SRAM
 ↓ ↘ word size
 # of words ↓
 units in bits!!

4×2 SRAM
 means
 4 words with
 2 bits each

- Look into the handout for an example 4×2 SRAM! (also on Canvas)

WE = write enable

OE = output enable

CS = chip select (if CS = 0 then this chunk of RAM does nothing)

* If we want to build large SRAMs the circuits become thin rectangles.

↳ We want squares. Let's put multiple words on one line.

$$8K \times 32 = 2^3 \cdot 2^{10} \cdot 2^5 \\ = 2^{18} \text{ bits total}$$

Square layout would have:

2^9 latches per side.


$$2^9 / \underbrace{2^5}_{\text{word size}} = 2^4 \text{ words in a line.}$$

* We still want a single word out of this!

* We will use part of the address to select row, then select word with the rest of the bits.

- * There are 8K words in the RAM.
- * Therefore there are 2^{13} things to choose from. The address will be 13 bits!

 - * Since we have 2^9 rows, we will use 9 of those address bits to select the row. The remaining 4 will select the word.



- * The most significant bits select the row!

Summary:

In an $n \times m$ SRAM:


- $\log_2 n$ address bits
- Cell array is $\sqrt{n \times m}$ rows by $\sqrt{n \times m}$ columns
- $\log_2 \sqrt{n \times m}$ bits to select row
- $\log_2 n - \log_2 \sqrt{n \times m}$ input mux
- m data bits

So in a $32K \times 8$ SRAM

- $2^5 \cdot 2^{10} = 2^{15}$, 15 address bits
- 2^9 rows
- 2^9 columns
- 9 bits to select row
- $15 - 9 = 6$ bits to select word
- 8 data bits

DRAM Cell

- Stores value in capacitor

 

- Stores 1 bit! Uses fewer transistors, than SRAM, thus cheaper.

To read:

- 1) wordline = 1
- 2) wait for capacitor to discharge
- 3) observe bitline.

* NOTE: Reading a DRAM cell destroys its value. You need to write the value you observed back.

To write:

- 1) wordline = 1
- 2) charge and hold bitline until capacitor is charged or discharged
- 3) wordline = 0 to store

* The capacitor will leak in about 10^{-3} seconds even if not read.

PRAM's periodically refresh themselves.

— END EXAM 2 —